32KB Upgrade for M100 and PC-8201

by Steve Adolph February 2010

- Use this upgrade if you can't get the custom OEM ram modules, and you want to upgrade to 32k in the M100, or 2x32k in the PC-8201
- This upgrade uses 62256 class of 32kB SRAM chips in 28 pin DIL packages
 - There are tons of different part numbers that fit this category
 - In general you want low power versions
 - The part you use should match the pinout shown in this document
- 3 Steps in the process
 - Step 1: Removal and/or de-activation of existing 8KB ram modules
 - Step 2: Installation of new 32KB ram chip(s)
 - Step 3: Installation of 74HC138 decoder to generate the chip select(s)

Preparation

- What you will need:
 - Xacto knife for cutting PCB traces
 - Some 5 minute epoxy or similar
 - One or two 62256 type ram chip
 - 74HC138 decoder chip
 - Solder, wire-wrap wire, wire strippers, pliers, philips screwdriver
 - Solder pump or solder wick for removing solder
- To get started:
 - Open the case, disconnect the top from bottom
 - Remove all socketed ram modules
 - Remove the motherboard from the case
 - Be careful to remember how to put it back together!

Step 1: PC-8201 ram disable


To disable the soldered-in ram-

- Disconnect IO/M from pin 1 of U1
 - Cut the track on the primary side of the board, near pin 1
 - Or, clip the pin at the chip, leaving a shoulder to solder to
- Solder a wire from pin 1 of U1 to pin 16 of U1 to tie cut signals to +5V
 - This disables the 74HC139 decoder, making the 4 downstream 74HC138 decoders inoperative as well.

77 7 8 70 20 6 70 77 0.022 7 77 0.022 7 77 0.022 7

Truth Table

In	puts		Outputs				
Enable	Sel	Select					
G	В	Α	Y0	Y1	Y2	Y3	
н)	Х	Х	Н	Н	Н	Н	
	L	L	L	Н	Н	н	
L	L	н	н	L	Н	н	
L	н	L	н	Н	L	н	
L	н	Н	н	Н	Н	L	

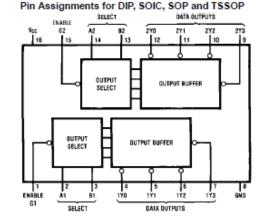


H = HIGH Level L = LOW Level X = Don't Care

Step 1: M100 ram disable


To disable the soldered in ram-

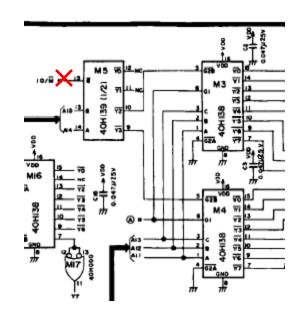- Disconnect IO/M from pin 15 of M5
 - Either cut a track, being careful to maintain other connections
 - Or, clip the pin at the chip, leaving a shoulder to solder to
- Solder a wire from pin 15 of M5 to pin 16 of M5 to tie cut signal to +5V
 - This disables the 74HC139 decoder, making the 2 downstream 74HC138 decoders inoperative as well.



Truth Table

In	puts		Outputs				
Enable	Select						
G	В	Α	Y0	Y1	Y2	Y3	
н)	Х	Х	Н	Н	Н	Н	
1	L	L	L	Н	Н	н	
L	L	н	н	L	Н	н	
L	н	L	н	Н	L	н	
L	н	Н	н	Н	Н	L	

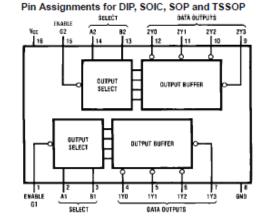

H = HIGH Level L = LOW Level X = Don't Care


62256 Ram chips

- 28 pin DIP package, see truth table below
- The /CS signal is a special signal in that it toggles between VB and GND, not +5 and GND. /CS signal is the only control that can put the chip in sleep mode, and is the only signal used to enable the device for a read/write
- /OE should be grounded in this application
- /WE should be = /WR signal in M100

Truth Table


_	CS	ŌE	WE	Mode	V _{CC} current	I/O pin	Reference cycle
	Н) x	x ,	Not selected	I _{SB} , I _{SB1}	High Z	
	L	L	н	Read	lcc	Dout	Read cycle No. 1-3
	L	н	L	Write	lcc	Din	Write cycle No. 1
	L	L	Ł	Write	Icc	Din	Write cycle No. 2

Note: x means H or L

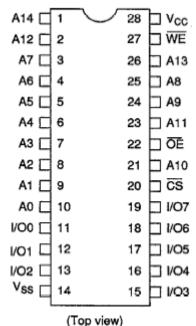


M100 Ram Module Socket

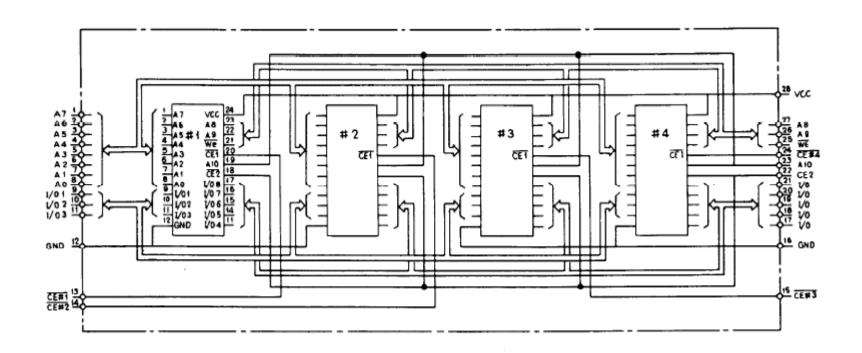- Lots of pins are in the right place, some are not
- For reference, the below diagram shows the pinout of the M100 ram module




Step 2: Preparation of the socket

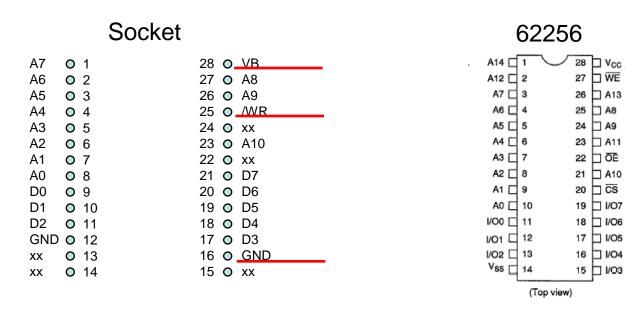

- solder a wire to
 - VB pin 28
 - /WR pin 25
 - pin 16 GND
- bend chip leads away from the socket so that the ram chip is clear to be inserted.

Step 2: Insert Ram chip in socket

62256 in socket

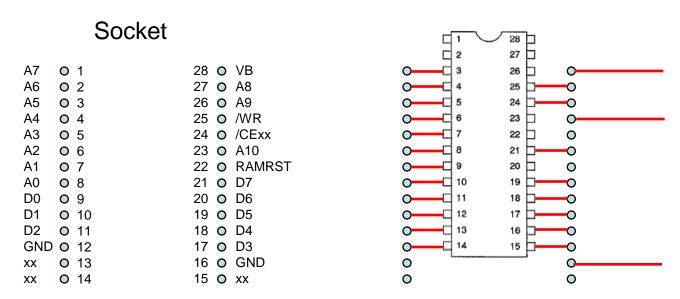

- Spread leads of ram chip to fit socket
- clip chip pins 1, 2, 28, 27, 26, 23, 22 and 20 at the shoulder, leave the stub
- bend stub up and away from the socket pin, so that access to both the socket pin and the ram stub pin is possible.
- insert ram chip(s) into ram module socket(s)
- you should still have three wires unconnected on socket pin 28, 25 and 16


Step 2: connect power and /WR

62256 in socket

	Socket		1 28
A7 A6 A5 A4 A3 A2 A1 A0 D0	O 1 0 2 0 3 0 4 0 5 0 6 0 7 0 8 0 9 0 10	28 O VB 27 O A8 26 O A9 25 O /WR 24 O /CExx 23 O A10 22 O RAMRST 21 O D7 20 O D6 19 O D5	1 28 27 27 3 26 3 26 3 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0
D2 GND xx xx	0 11	18 O D3 18 O D4 17 O D3 16 O GND 15 O xx	13 16 0 14 15 0

- Vb -solder lead from pin 28 of socket to pin 28 of ram chip
- /WE solder lead from pin 25 of socket to pin 27 of ram chip
- /OE solder lead from pin 16 of socket to pin 22 of ram chip

Step 2: connect missing address lines

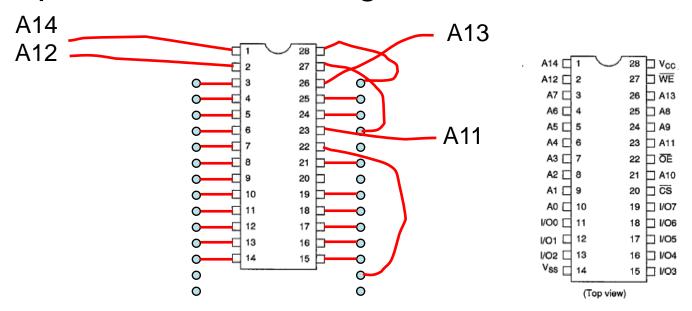

Line	M100 location	PC-8201 location (note – connect on underside of PCB)
A14	pin 14 of M5	Pin 2 U1
A13	pin 3 of M4	Pin 3 U4
A12	pin 2 of M4	Pin 2 U4
A11	pin 1 of M4	Pin 1 U4

PC-8201 note: make sure these wires stay clear of case, when reassembling.

Step 3: generating /CS1 (and /CS2)

- Use a 74HC138 decoder to generate /CS1, /CS2
 - You can purchase them on eBay, or otherwise, or
 - you can de-solder and reused one of the unused 74HC138s.
 - Unused means no ram chips hanging off of it!
 - In PC8201, there are 3 spares U3, U4, U5.
 - In 8k M100, there is one spare M3
 - No spares in 24k M100.

Proper /CS requirements

- it will toggle between +5V and GND during normal operation
- It will be pinned at Vb when the chip is in protect/standby mode
 - This happens when reset is hit, or the machine is off
- This is done by powering the 74HC138 from Vb.

Step 3: location for 74HC138

Preparation


- You will want to glue the chip on it's back so the pins are up in the air
- Bend the chip leads gently outwards so that they are more gull-winged, and don't stick up quite so high.

Placement

- in both models, you can place the chip on the board between the socket pins of an unused ram module socket.
 - In PC-8201, it is easier to place it on the "internal" side, not in the expansion bay.
 - In the M100, it must be placed internally.

74HC138 decoder

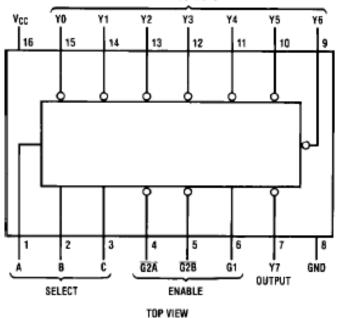Pin Assignment for DIP, SOIC, SOP and TSSOP DATA OUTPUTS




Truth Table

	Inputs							Out	puts			
	Enable Select			\neg								
G1	G2 (Note 1)	С	В	Α	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
Х	Н	Х	Х	Х	н	Н	Н	Н	Н	Н	Н	Н
L	X	Х	X	X	н	Н	Н	Н	Н	Н	Н	н
н	L	L	L	L	L	Н	Н	Н	Н	Н	Н	Н
н	L	L	L	Н	н	L	Н	Н	Н	Н	Н	н
Н	L	L	Н	L	н	Н	L	Н	Н	Н	Н	Н
н	L	L	Н	Н	н	Н	Н	L	Н	Н	Н	н
н	L	н	L	L	н	Н	Н	Н	L	Н	Н	Н
н	L	н	L	Н	н	н	Н	Н	Н	L	Н	н
н	L	н	Н	L	н	н	Н	Н	Н	Н	L	н
н	L	н	Н	Н	н	Н	Н	Н	Н	Н	Н	L

H = HIGH Level, L = LOW Level, X = don't care

Note 1: G2 = G2A+G2B

Logic Diagram

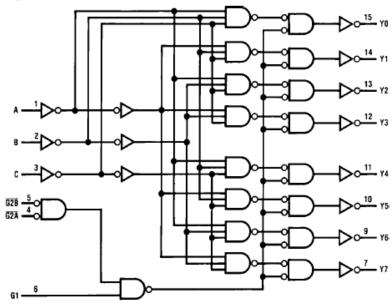

Step 3: 74HC138 connections

74HC138	M100	PC-8201
1, A	A15 (pin 13 M5)	A15 (pin 12 U23)
2, B	GND (pin 12 any ram socket)	/STDRAM (pin 5 U3)
3, C	Vb (pin 28 any ram socket)	/BANK2 (pin 5 U5)
4, /G2A	RAMRST (pin 22 any ram socket)	/POWER (pin 22 any ram socket)
5, /G2B	IO/M (pin 15 M5)	IO/M (pin 1 U1)
6, G1	A* (pin 6 M4)	E (pin 6 U3)
10, /CS1	Connect to 62256 /CS	Connect to 62256 /CS, bank 1
12, /CS2	N/A	Connect to 62256 /CS, bank 2
8, GND	GND (pin 12 any ram socket)	GND (pin 12 any ram socket)
16, Vcc	Vb (pin 28 any ram socket)	Vb (pin 28 any ram socket)

Finishing up:

- Glue down any wires that need to be tacked in place
- Reassemble the unit
- Test it out/debug as needed

